

# Problem set

## Analysis of filters with complex impedance

For each of the circuits in the table, figure out the complex number that represents the ratio of the output voltage divided by the input voltage. Write your final result in the tables. For each circuit in the table, create a plot of the magnitude of this complex number as a function of frequency. Put both the magnitude and frequency on a logscale. For each circuit use:

- $R_1 = 1 \text{ k}\Omega$   $C_1 = 1 \mu\text{F}$
- $R_2 = 10 \text{ k}\Omega$   $C_2 = 0.1 \mu\text{F}$




log log


Remember, the impedance of a resistor and capacitor are

- $Z_R = R$
- $Z_C = \frac{1}{j\omega C}$

log scale?

what is frequency?

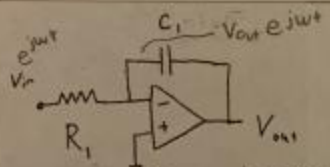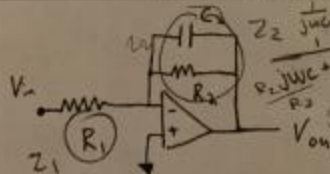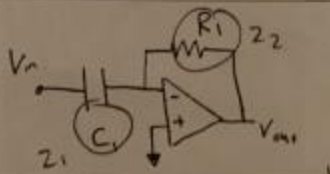 <p>Low Pass</p>	$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$
	$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \frac{R_2}{R_1 + \frac{R_2}{j\omega C_2 R_2 + 1}}$
 <p>High Pass</p>	$\frac{V_{out}}{V_{in}} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC}$

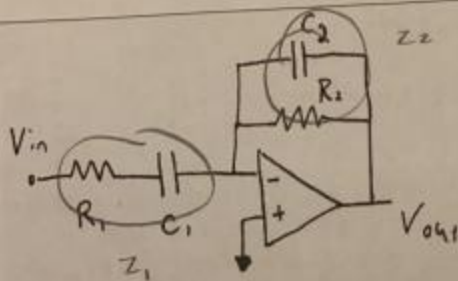


$$Z_2 = \frac{R_2}{j\omega C_2 R_2 + 1}$$

$$\frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$
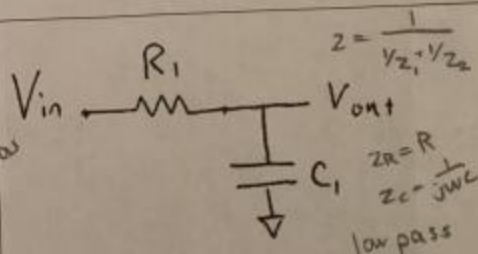
$$\frac{\frac{R_2}{j\omega C_2 R_2 + 1}}{R_1 + \frac{1}{j\omega C_1} + \frac{R_2}{j\omega C_2 R_2 + 1}}$$




$$V_{out} = V_{in} \frac{R_1}{R_2 + R_1} \quad Z_2 = \frac{1}{R_1 j\omega C_1 + 1}$$


$$V_{out} = V_{in} \frac{Z_2}{Z_1 + Z_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

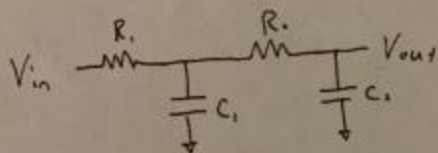
$$\frac{\frac{1}{j\omega C_1}}{R + \frac{1}{j\omega C_1}}$$


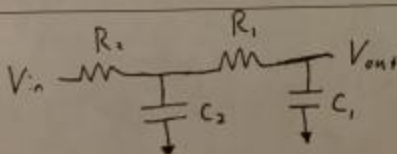
$$Z_R = \frac{1}{R_1 j\omega C_1 + 1} + \frac{1}{R_2 j\omega C_2 + 1}$$



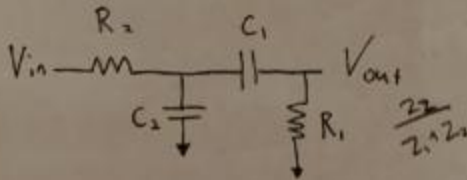
$$Z = \frac{1}{R_2 j\omega C_2 + 1} + \frac{1}{R_1 j\omega C_1 + 1}$$




$$Z_R = \frac{1}{R_2 j\omega C_2 + 1} + \frac{j\omega C_1}{1 + j\omega C_1 R_1}$$

$$C_1 \quad \frac{R_1}{\frac{1}{j\omega C_1} + R_1}$$


**First Circuit**

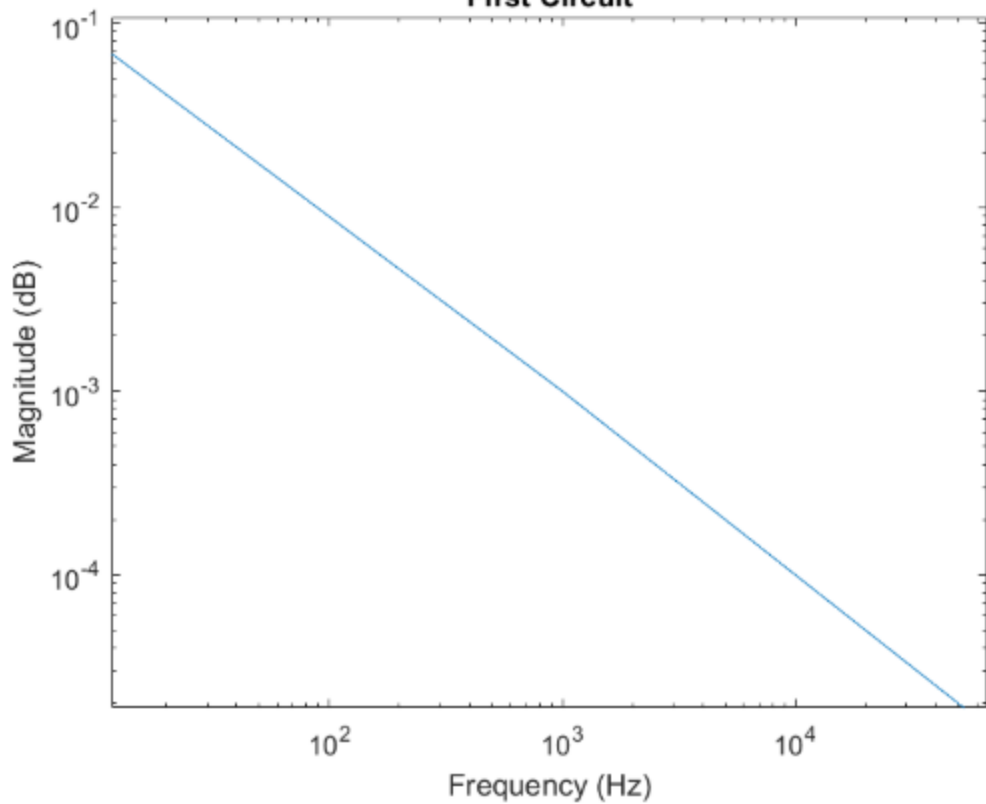


**Second Circuit**

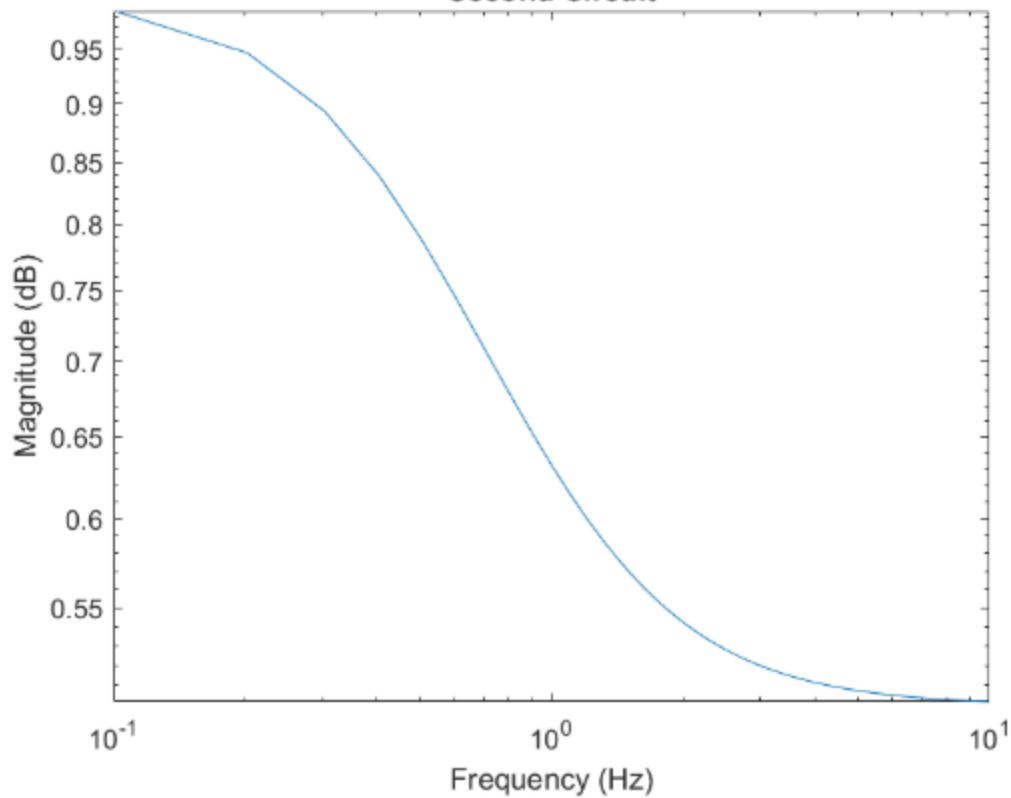


**Third Circuit**

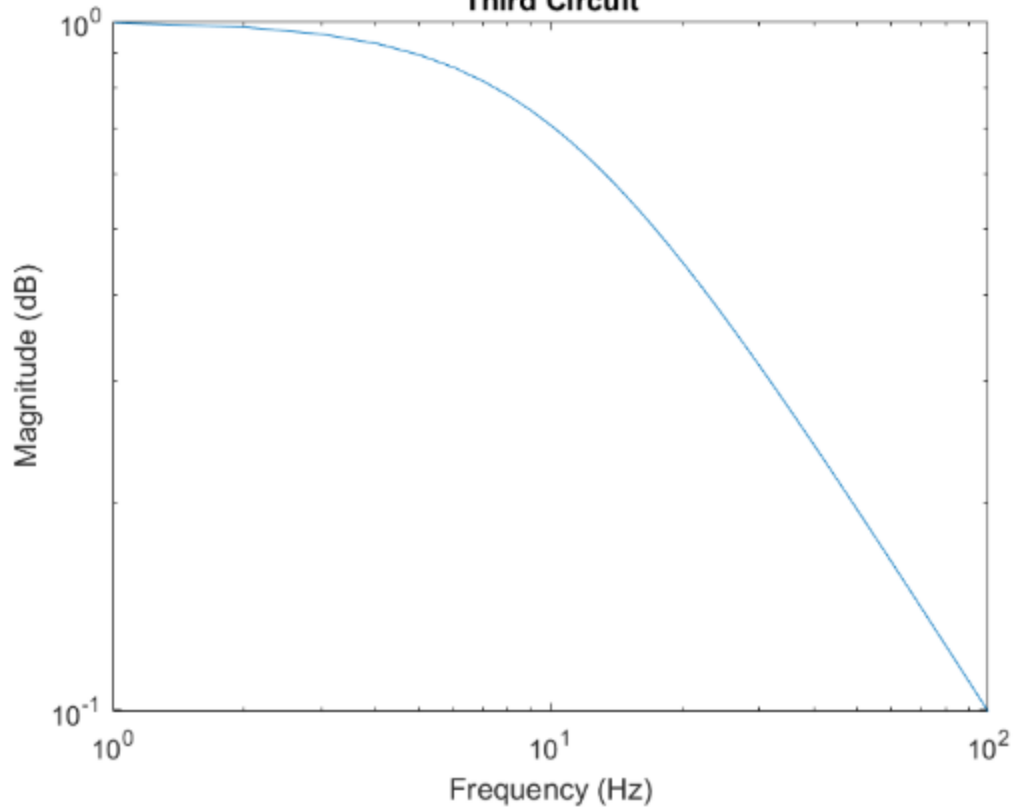


**Fourth Circuit**

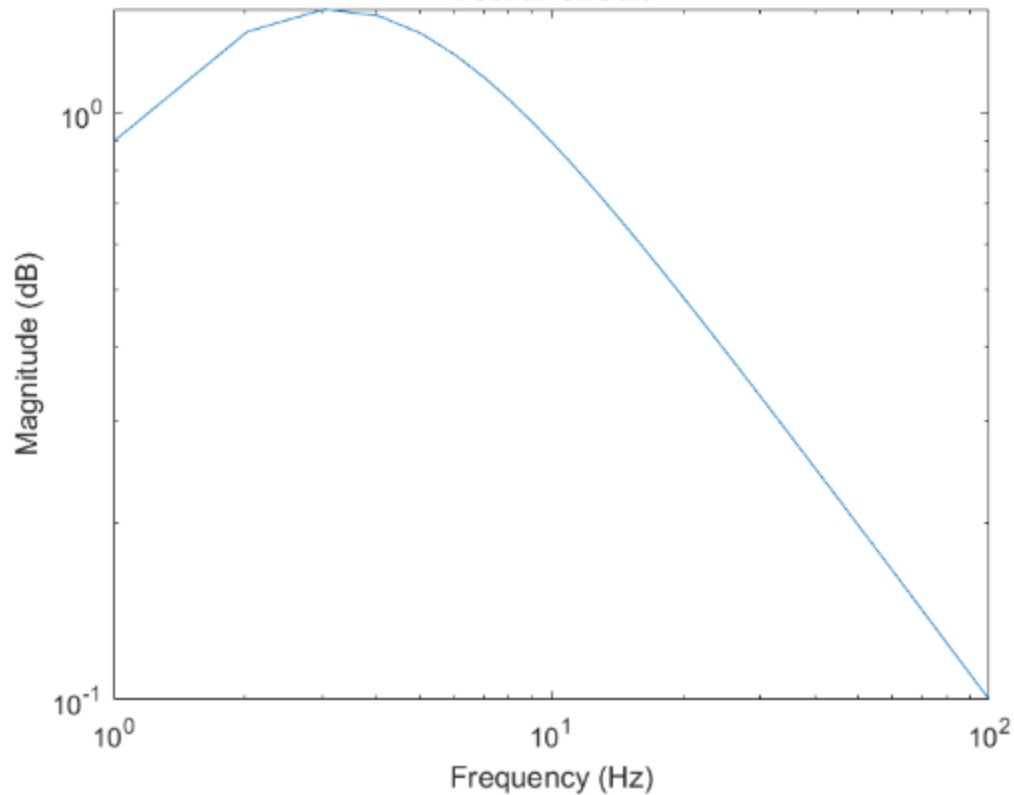

**Fifth Circuit**

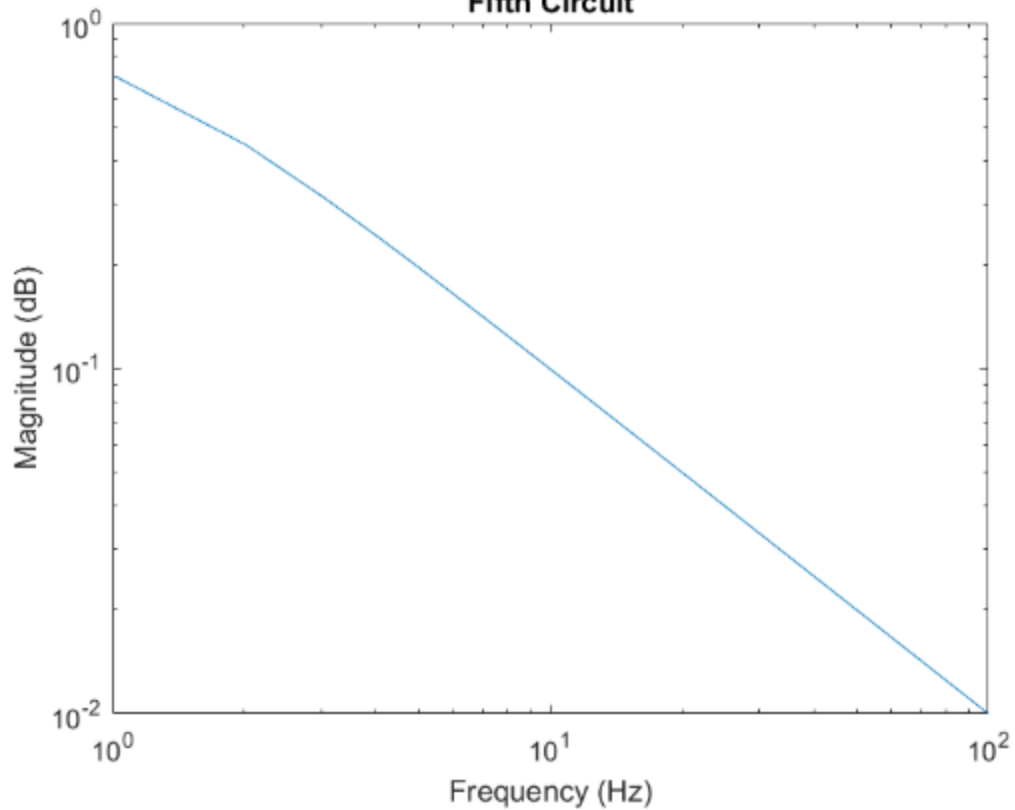


**Sixth Circuit**

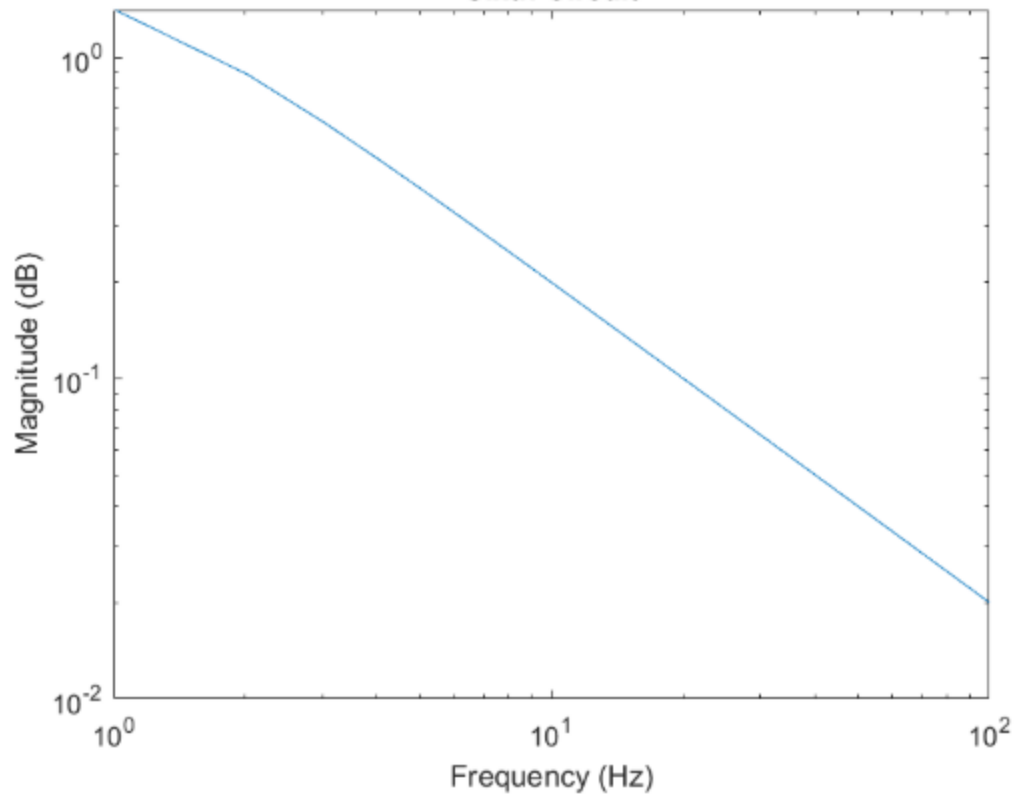



**Seventh Circuit**

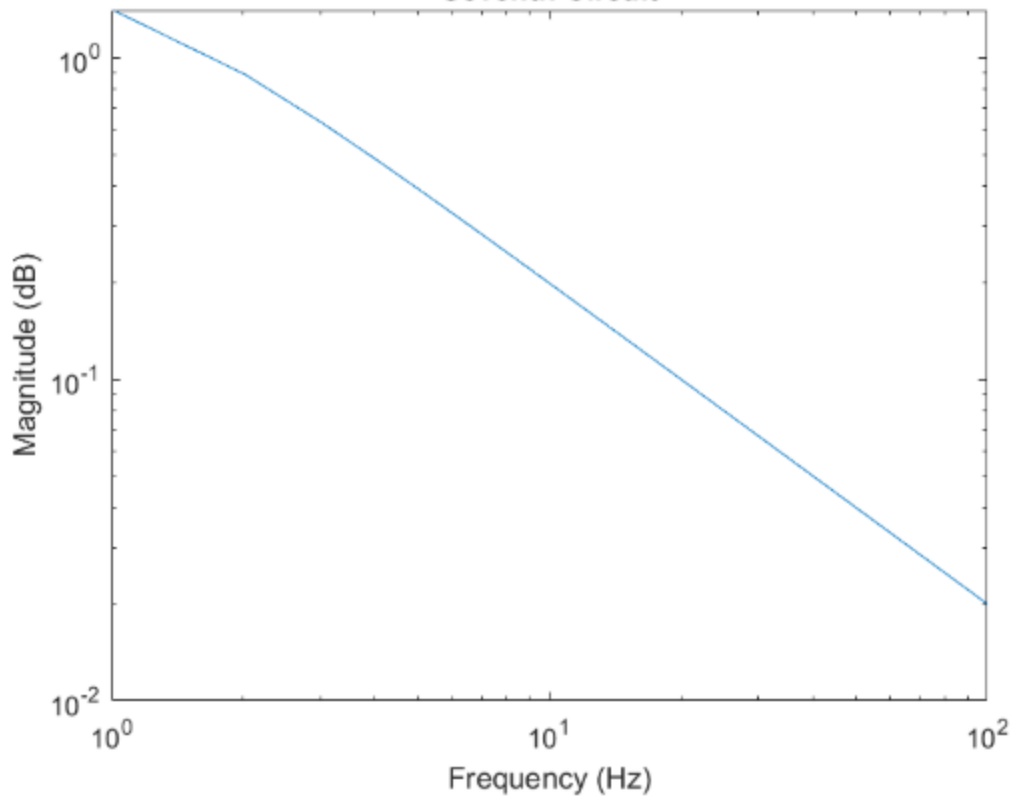

**Eighth Circuit**

